 


Chapter 8.


Sequential Circuit Analysis and Timing

Acknowledgments. Some slides and/or picture in the following are adapted from
Digital Design: Principles and Practices (3rd Edition) by John F. Wakerly
and David E. Orin class slides


Various Types of FFs



Input D	Next state
0	0
1	1

 


J	K	Next state
0	0	Q
0	1	0
1	0	1
1	1	Q'

 


Input EN	Next state
0 at rising edge T	Q
1 at rising edge T	Q'

Analysis of Clocked Synchronous State Machines

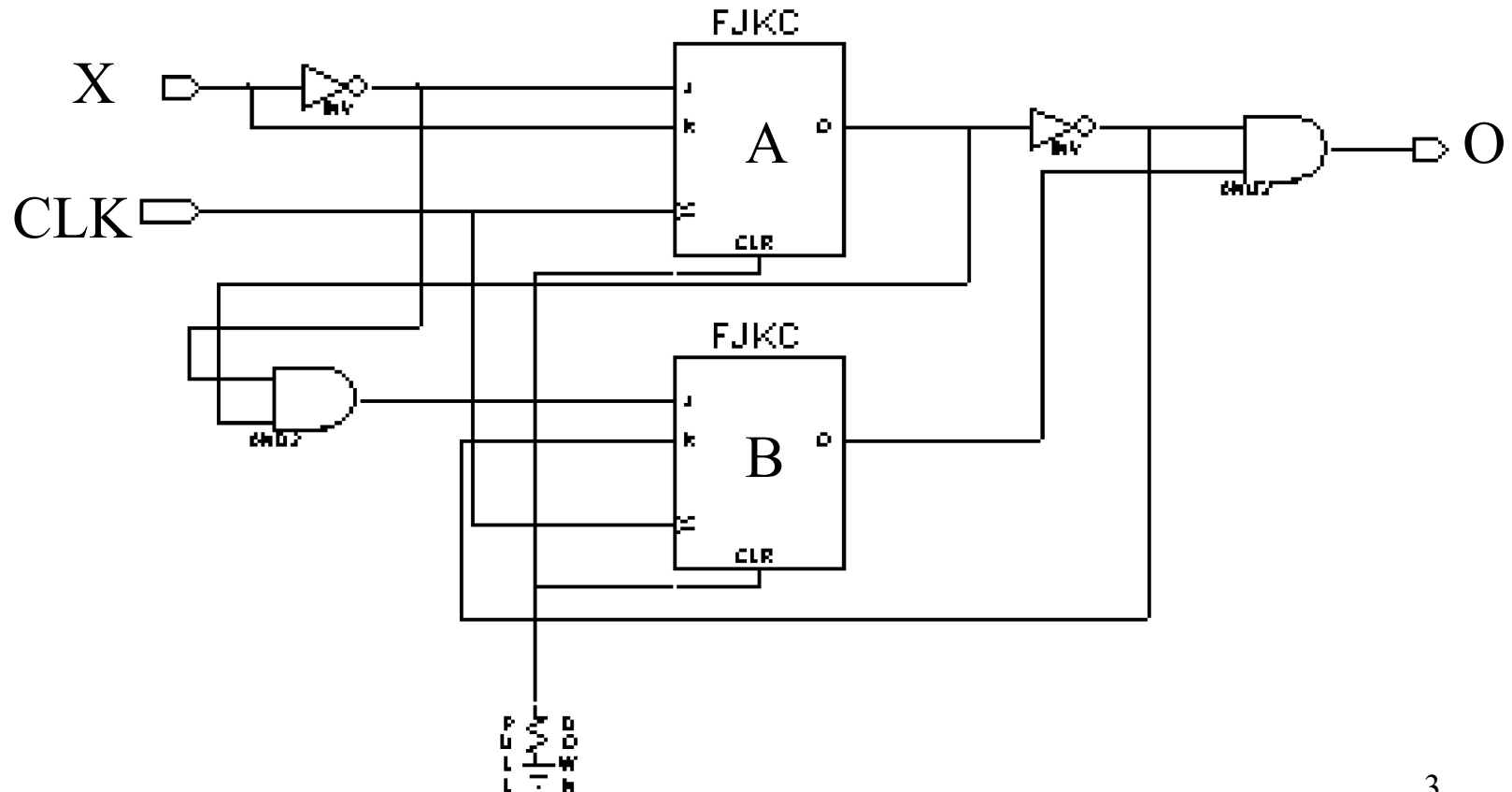- Begin with circuit
- End with state diagram – word description
- 3 step approach



Synchronized Operation With CLK

 

Step 1: Excitation and Output Equations

- **Derive Excitation and Output Equations from the schematic**

$$J_A = \overline{X}, K_A = X,$$

$$J_B = Q_A \overline{X}, K_B = \overline{Q_A},$$

$$O = \overline{Q_A} Q_B$$

Step 2: State/Output Table

C.S. Input Output				C.S. Input				Excitation				C.S. Input				N.S	
QB	QA	X	O	QB	QA	X		JB	KB	JA	KA	QB	QA	X		QB	QA
0	0	0	0	0	0	0		0	1	1	0	0	0	0		0	1
0	0	1	0	0	0	1		0	1	0	1	0	0	1		0	0
0	1	0	0	0	1	0		1	0	1	0	0	1	0		1	1
0	1	1	0	0	1	1		0	0	0	1	0	1	1		0	0
1	0	0	1	1	0	0		0	1	1	0	1	0	0		0	1
1	0	1	1	1	0	1		0	1	0	1	1	0	1		0	0
1	1	0	0	1	1	0		1	0	1	0	1	1	0		1	1
1	1	1	0	1	1	1		0	0	0	1	1	1	1		1	0

Output Table

Excitation Table


Transition Table

Step 2: State/Output Table

P.S.		Input		Output	Excitation				N.S.	
QB	QA	X		O	JB	KB	JA	KA	QB	QA
a	0	0	0	0	0	1	1	0	0	1
	0	0	1	0	0	1	0	1	0	0
b	0	1	0	0	1	0	1	0	1	1
	0	1	1	0	0	0	0	1	0	0
c	1	0	0	1	0	1	1	0	0	1
	1	0	1	1	0	1	0	1	0	0
d	1	1	0	0	1	0	1	0	1	1
	1	1	1	0	0	0	0	1	1	0

Step 2: State/Output Table (Cont.)


C.S.	X	O	N.S.
a	0	0	b
a	1	0	a
b	0	0	d
b	1	0	a
c	0	1	b
c	1	1	a
d	0	0	d
d	1	0	c

 


State	X	
	0	1
a	b,0	a,0
b	d,0	a,0
c	b,1	a,1
d	d,0	c,0

Step 3: State Diagram

 - Can you tell what this machine is doing?




Example

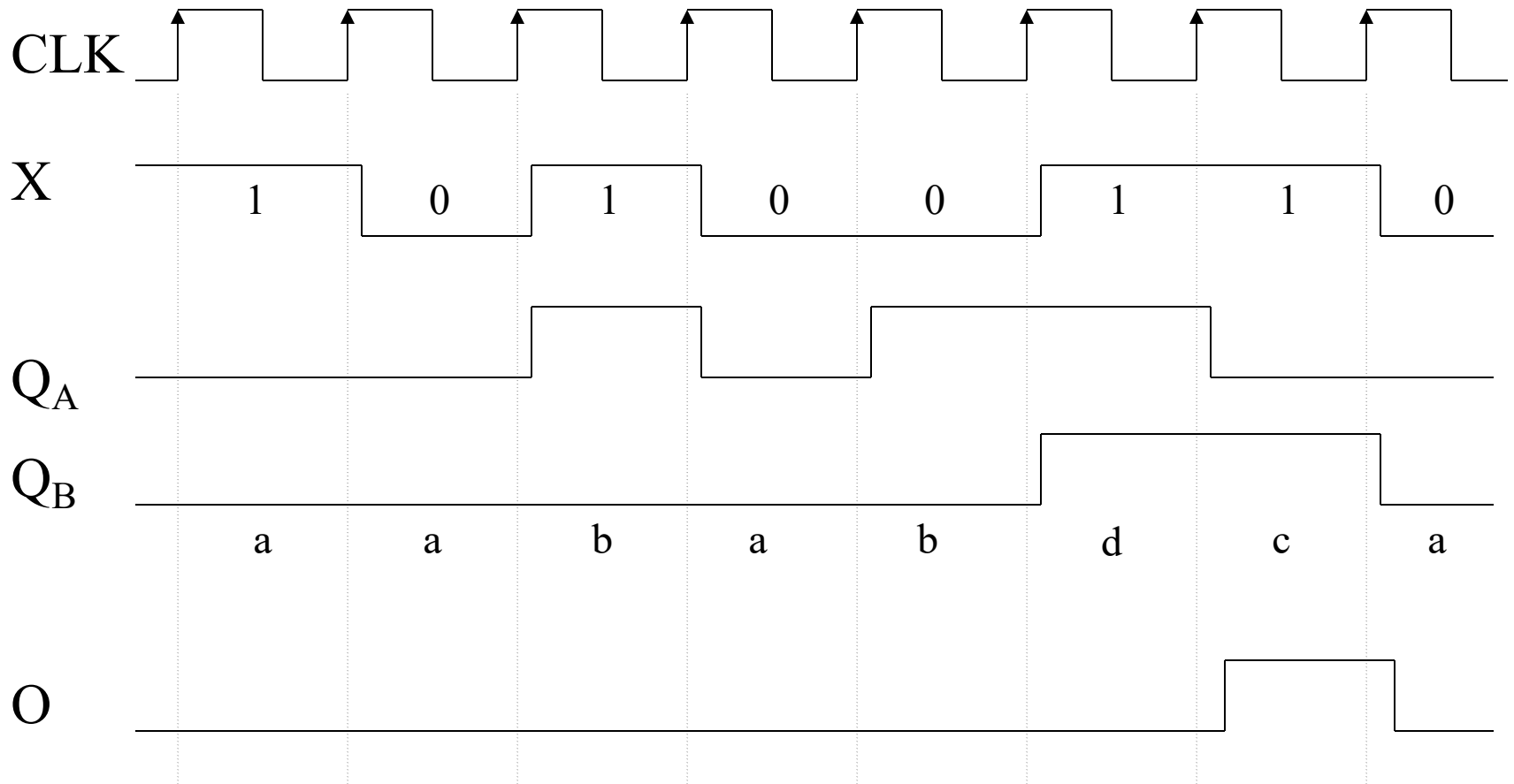


Timing

 
- **If this circuit is to work with a larger system, what are the timing requirements? – Timing specification**




Metastability

 



Metastability of a sequential logic

 

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

 


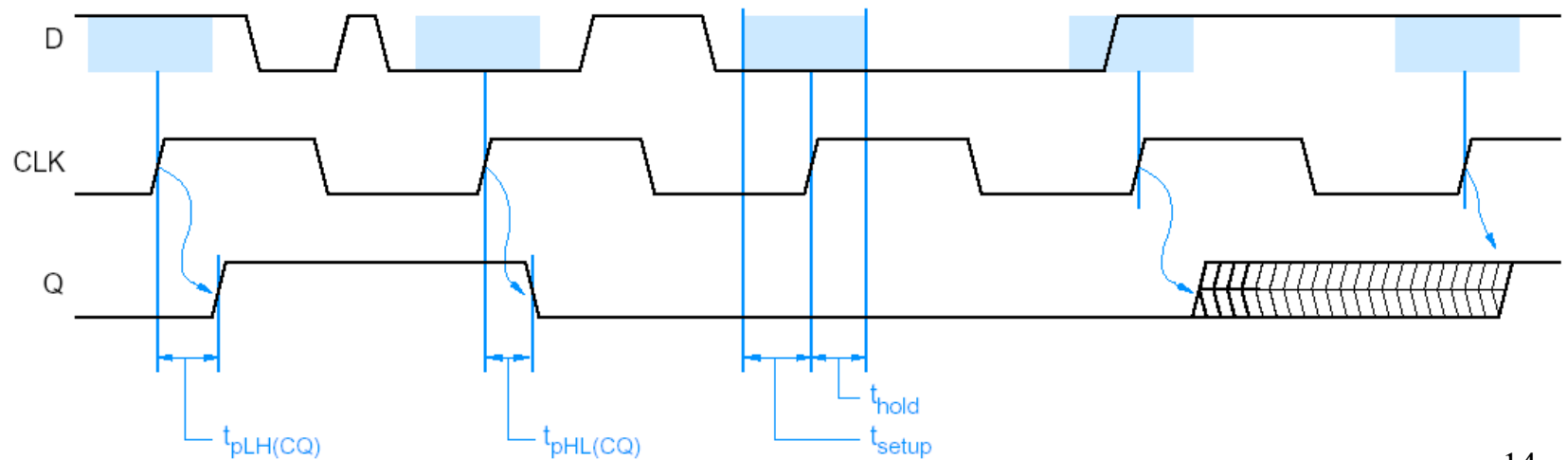 Setup & Hold Times of Sequential Components (e.g. D-ff)




Maximum CLK frequency

- How fast can the circuit work?

 

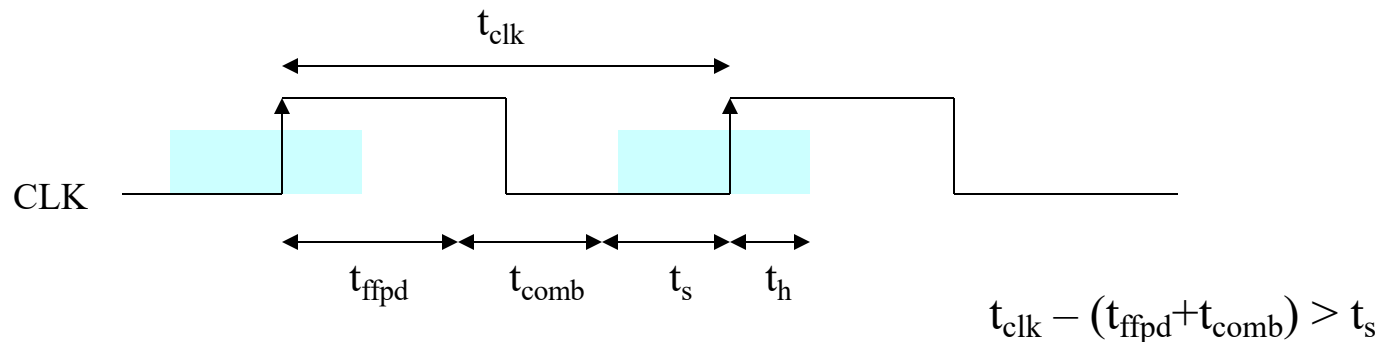- Assume inputs are ready at the right time



Maximum CLK frequency

- Timing specs for 74LS parts

	Propagation delay	Setup time	Hold time	Max freq.
74LS04 (Inverter)	$t_{pLH} = 15 \text{ ns}$ $t_{pHL} = 15 \text{ ns}$	N/A		
74LS08 (AND)	$t_{pLH} = 15 \text{ ns}$ $t_{pHL} = 20 \text{ ns}$	N/A		
74LS109 (JK f/f)	$t_{pLH} = 25 \text{ ns}$ $t_{pHL} = 40 \text{ ns}$	$t_s = 35\text{ns}$ for H data in $t_s = 25\text{ns}$ for L data in	$t_h = 5\text{ns}$	25 Mhz


- Find the worst case delay path

- Sum up worst case component delay, independent of transition direction
H->L, L->H
- 109 t_p ->08 t_p ->109 t_{setup} : $40 + 20 + 35 = 95 \text{ ns}$
- 109 t_p ->04 t_p ->109 t_{setup} : $40 + 15 + 35 = 90 \text{ ns}$


- Max $f_{\text{clk}} = 1/95\text{ns} = 10.5 \text{ Mhz}$

Setup and Hold time specifications on X

- t_s for X

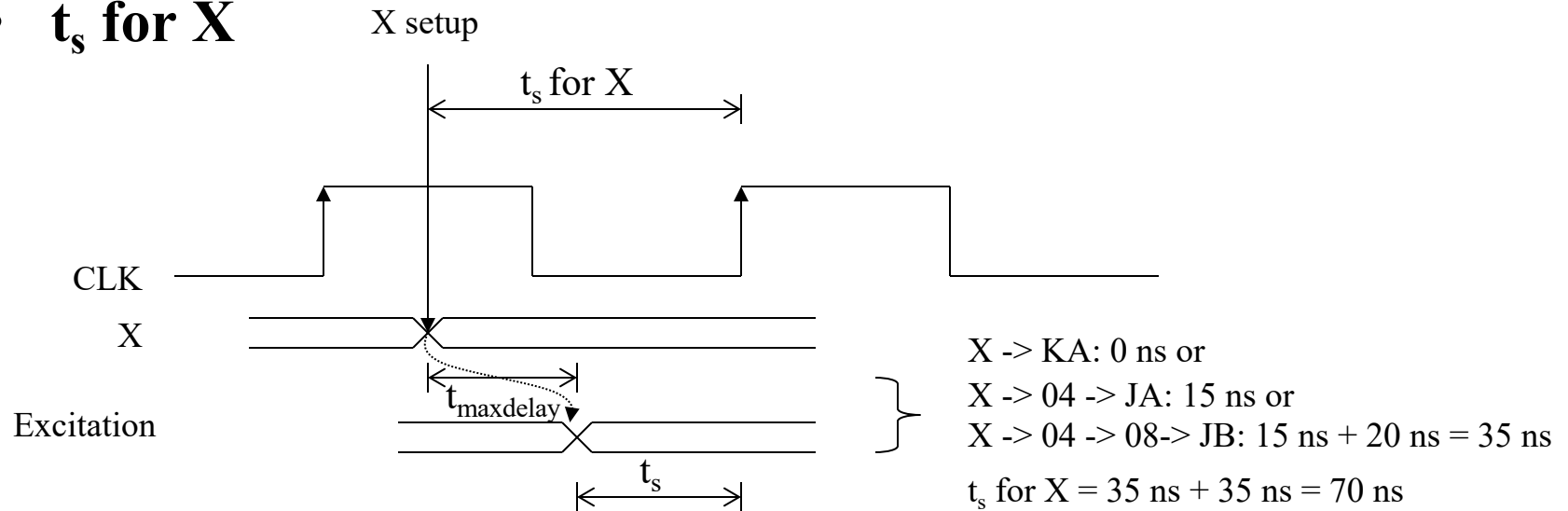

- t_h for X

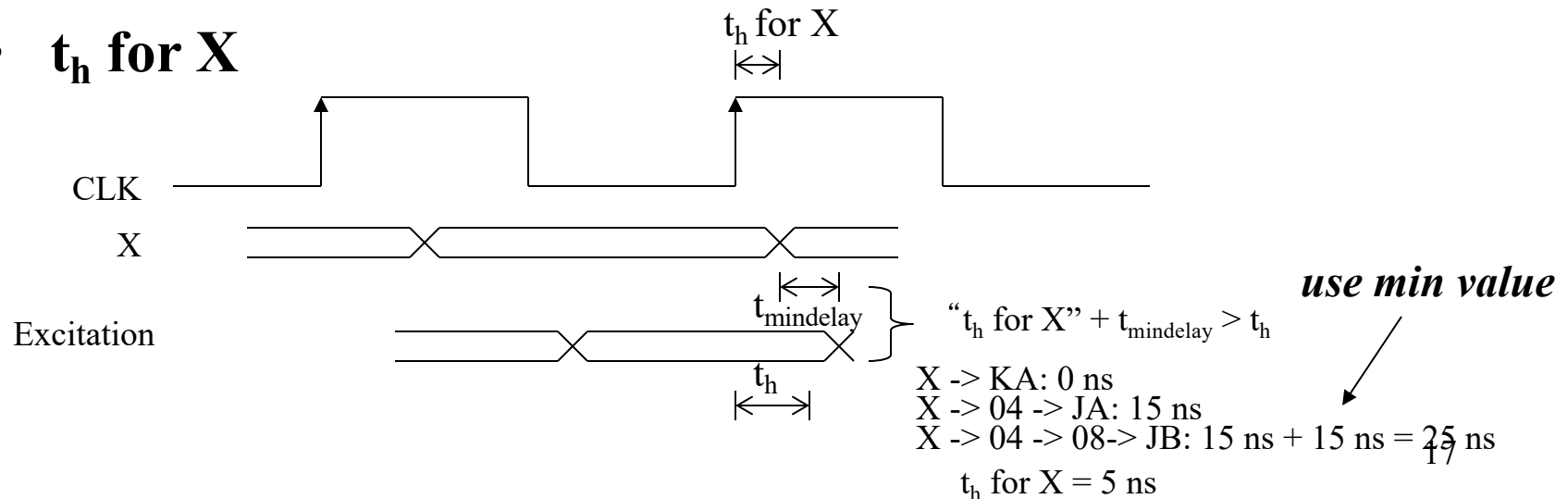

Propagation delay

- **X -> O: N/A (Applicable only for Mealy type output)**
- **CLK -> O:**
 - $tp_{LH} = \max (tp_{LH} '109 + tp_{LH} '08, tp_{HL} '109 + tp_{LH} '04 + tp_{LH} '08)$
 $= \max (25 \text{ ns} + 15 \text{ ns}, 40 \text{ ns} + 15 \text{ ns} + 15 \text{ ns}) = 70 \text{ ns}$
 - $tp_{HL} = \max (tp_{HL} '109 + tp_{HL} '08, tp_{LH} '109 + tp_{HL} '04 + tp_{HL} '08)$
 $= \max (40 \text{ ns} + 20 \text{ ns}, 25 \text{ ns} + 15 \text{ ns} + 20 \text{ ns}) = 60 \text{ ns}$


Final timing spec for our circuit

	Propagation delay	Setup time	Hold time	Max freq.
Our circuit	$t_{pLH} = 70 \text{ ns}$ $t_{pHL} = 60 \text{ ns}$	$t_s = 70 \text{ ns}$	$t_h = 5 \text{ ns}$	10.5 Mhz


- **This spec will be used for analyzing timing of a larger system containing our circuit as a component.**

Quiz

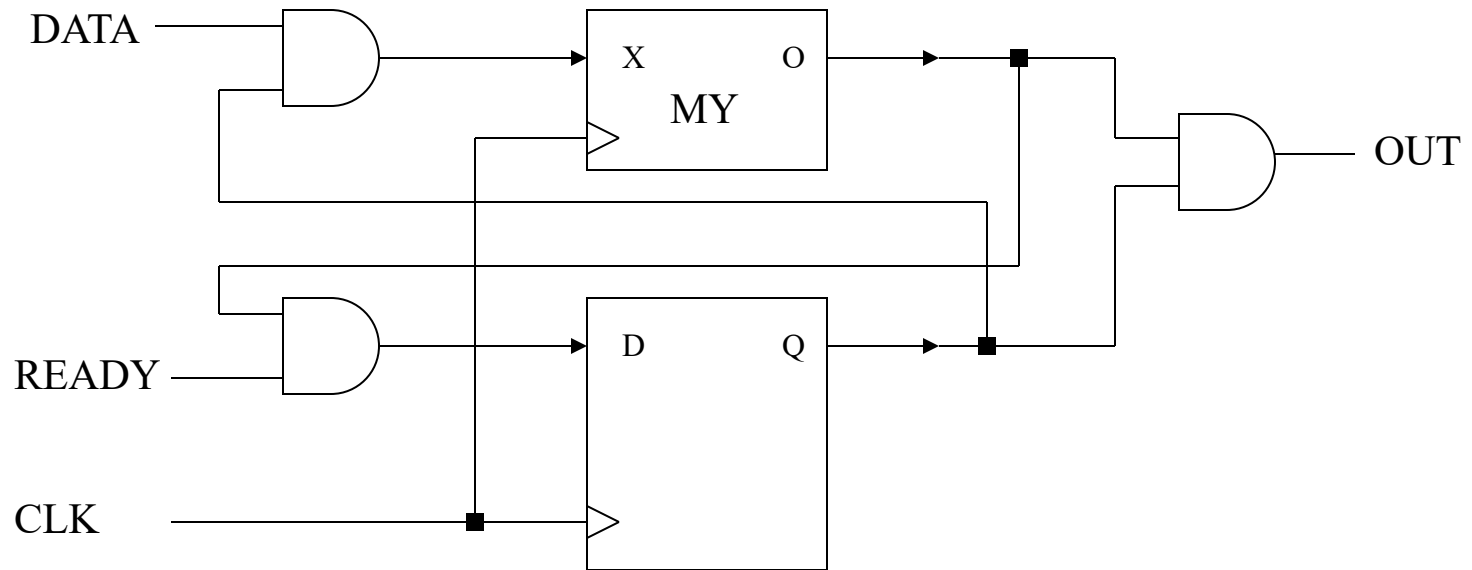
- **What is the maximum clock frequency of the following circuit?**



Can you tell what this guy is doing?

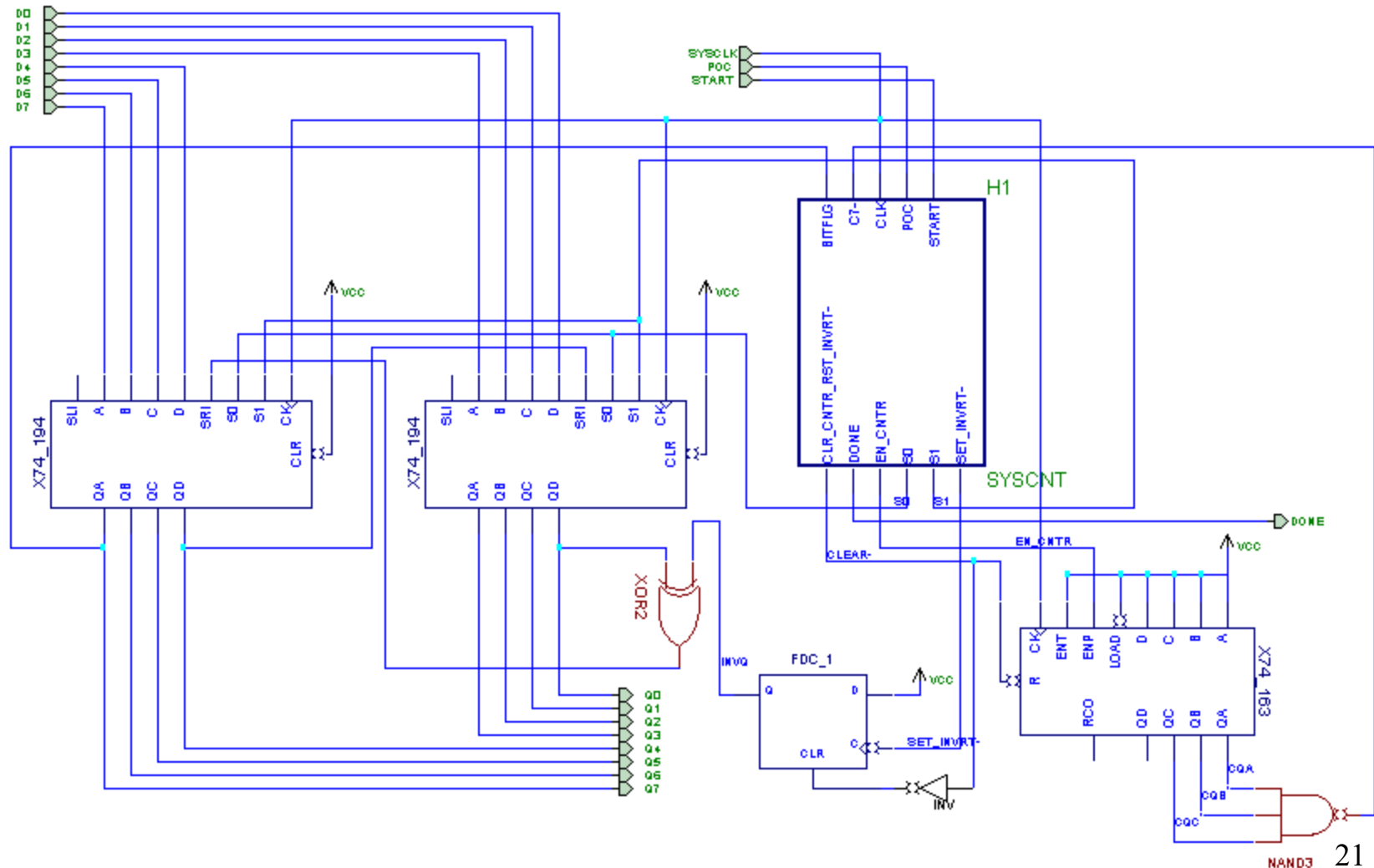


SYSCNT

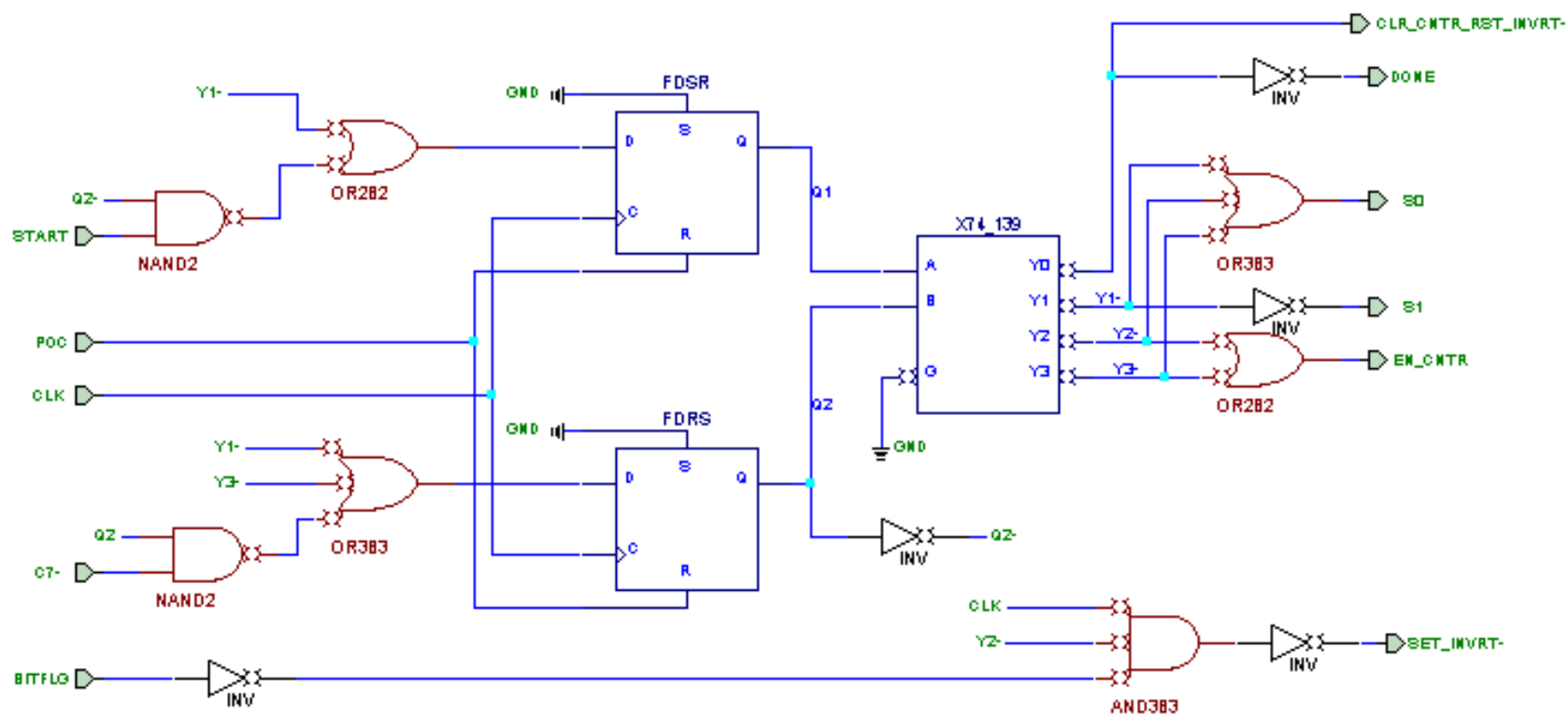


Bubble-to-bubble approach


(a)

 


(b)

 

(c)

 


(d)

 


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Proper use of bubbles and naming

 
- **Name of a signal:** Help understanding the circuit like meaningful variable names in C programs (READY, GO, ENABLE, REQUEST, etc)
- **Active High or Active Low** (to take advantage of gate implementation, e.g., NOR is faster than OR)
- **Use the bubble to represent Active Low signal and its name has “_L” or “-”** (e.g., READY_L or READY-)




(a)

 

(b)

 





(c)

 

(d)

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Examples

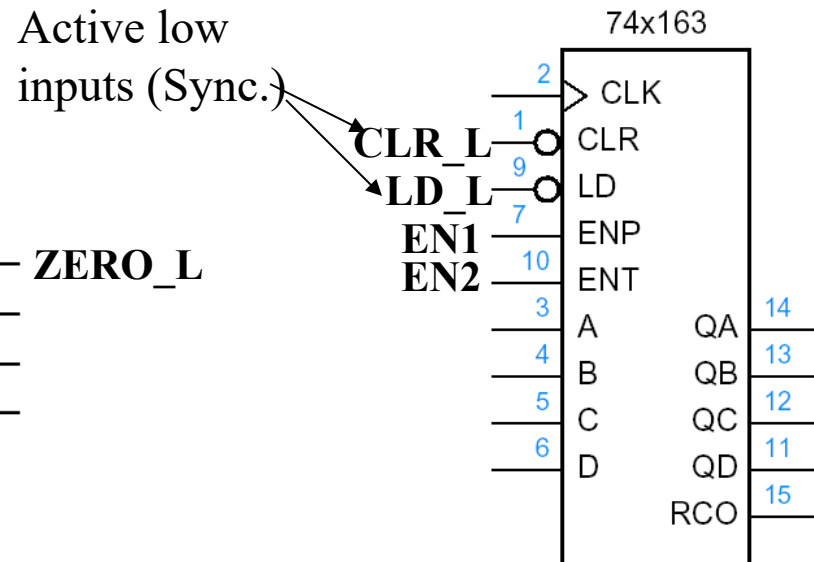   

MSI Chips

(used in our 2's complement machine)

Read: 8.4, 8.5, 6.4

(3rd Edition 8.4, 8.5, 5.4)

74LS163

- 4-bit, synchronous, parallel load, binary counter

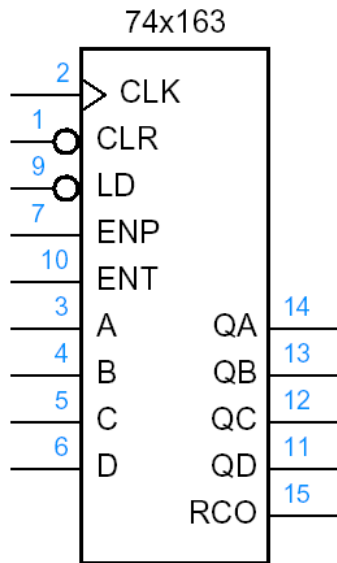


Table 8-11 State table for a 74x163 4-bit binary counter.


Inputs				Current State				Next State			
CLR_L	LD_L	ENT	ENP	QD	QC	QB	QA	QD*	QC*	QB*	QA*
0	x	x	x	x	x	x	x	0	0	0	0
1	0	x	x	x	x	x	x	D	C	B	A
	1	1	0	x	x	x	x	QD	QC	QB	QA
	1	1	x	0	x	x	x	QD	QC	QB	QA
	1	1	1	1	0	0	0	0	0	0	1
	1	1	1	1	0	0	1	0	0	1	0
	1	1	1	1	0	0	1	1	0	1	1
	1	1	1	1	0	0	1	1	0	1	0
	1	1	1	1	0	1	0	0	0	1	1
	1	1	1	1	0	1	0	1	0	1	0
	1	1	1	1	0	1	1	0	0	1	1
	1	1	1	1	0	1	1	1	0	0	0
	1	1	1	1	1	0	0	0	1	0	1
	1	1	1	1	1	0	0	1	0	1	0
	1	1	1	1	1	0	1	0	1	0	1
	1	1	1	1	1	1	0	0	1	1	0
	1	1	1	1	1	1	0	1	1	1	1
	1	1	1	1	1	1	1	0	0	0	0

RCO

0


8 bit counter using 74LS163 ?

- Cascading using RCO

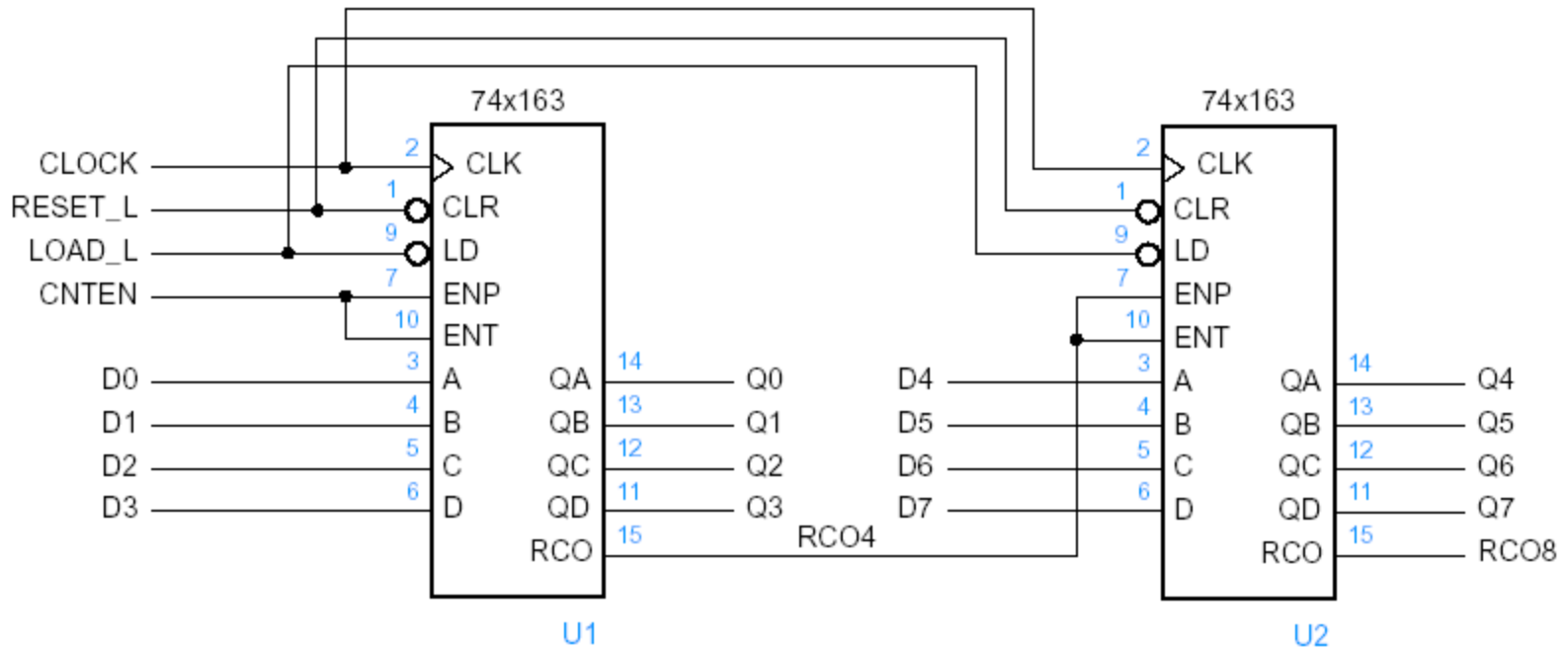

74LS194

 
- 4-bit, parallel in, parallel out, bi-directional shift register



Function	Inputs		Next state			
	S1	S0	QA*	QB*	QC*	QD*
Hold	0	0	QA	QB	QC	QD
Shift right	0	1	RIN	QA	QB	QC
Shift left	1	0	QB	QC	QD	LIN
Load	1	1	A	B	C	D

74LS139

- **Dual 2-to-4 Decoder**

 

<i>Inputs</i>			<i>Outputs</i>			
G_L	B	A	Y3_L	Y2_L	Y1_L	Y0_L
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

74LS138

- 3 Enables, 3-to-8 Decoder

 



Table 5-7 Truth table for a 74x138 3-to-8 decoder.

Inputs						Outputs							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1

Applications of Decoder

- **Address decoder**

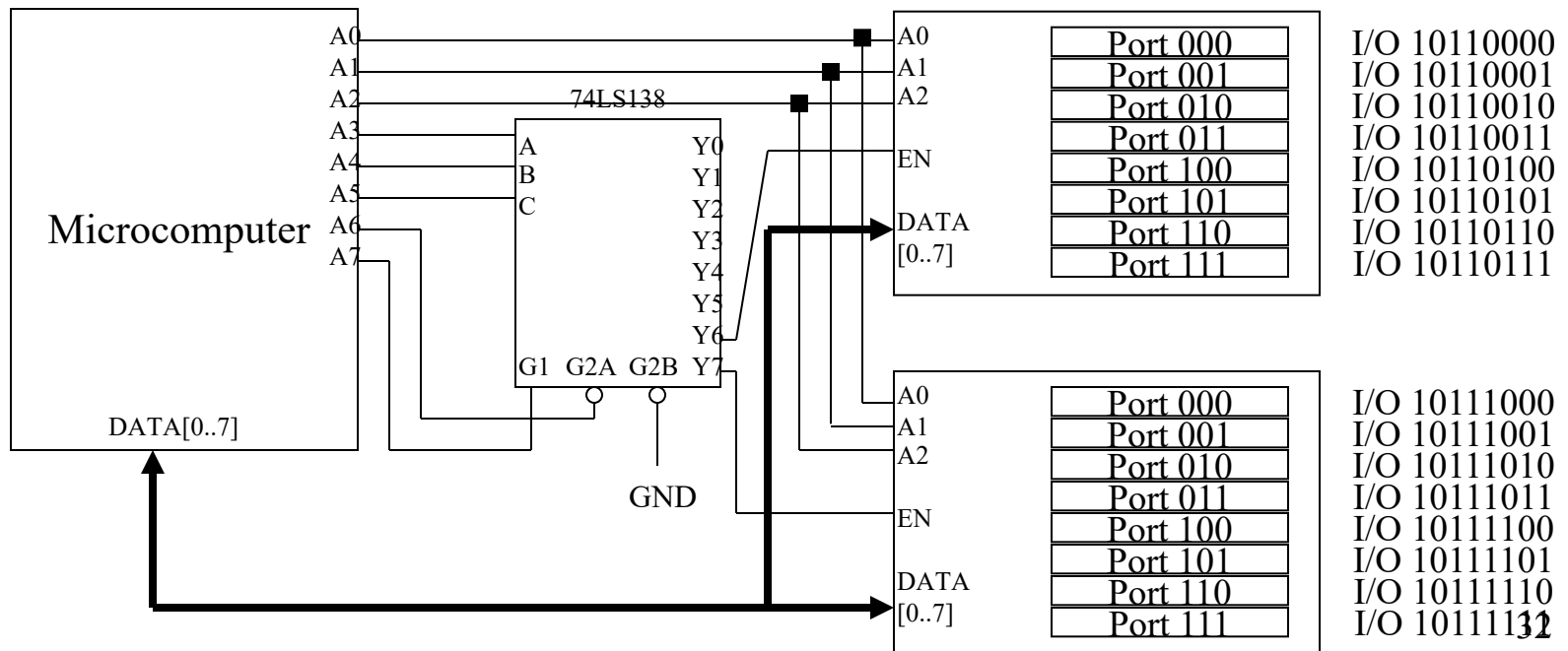
- In microcomputers, an I/O address is 8 bits so that there are 256 unique device addresses.
- How to make 16 I/O ports of two I/O chips (8 ports of each) to the following I/O mapped addresses?



Applications of Decoder

- Cascading**

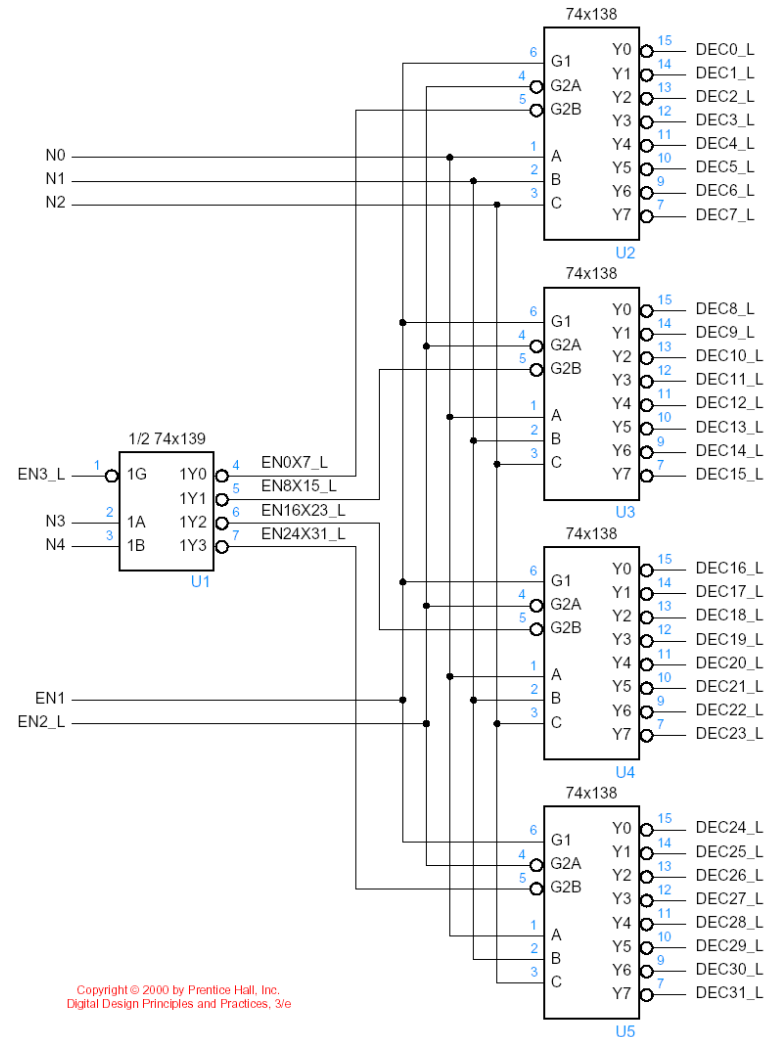
- Cascade small decoders for longer bits decoding
- How to make 5-to-32 decoder (with 3 enables EN1, EN2-, EN3-) using 74LS138 and 74LS139?



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e


Applications of Decoder

- Use as a Demultiplexer

 


- Use in combinational logic design

 
- Use a 74LS138 to implement $F = D\bar{E}\bar{F}(AB + \bar{A}\bar{B}\bar{C})$



		BA			
		00	01	11	10
C	0	1	0	1	0
	1	0	0	1	0

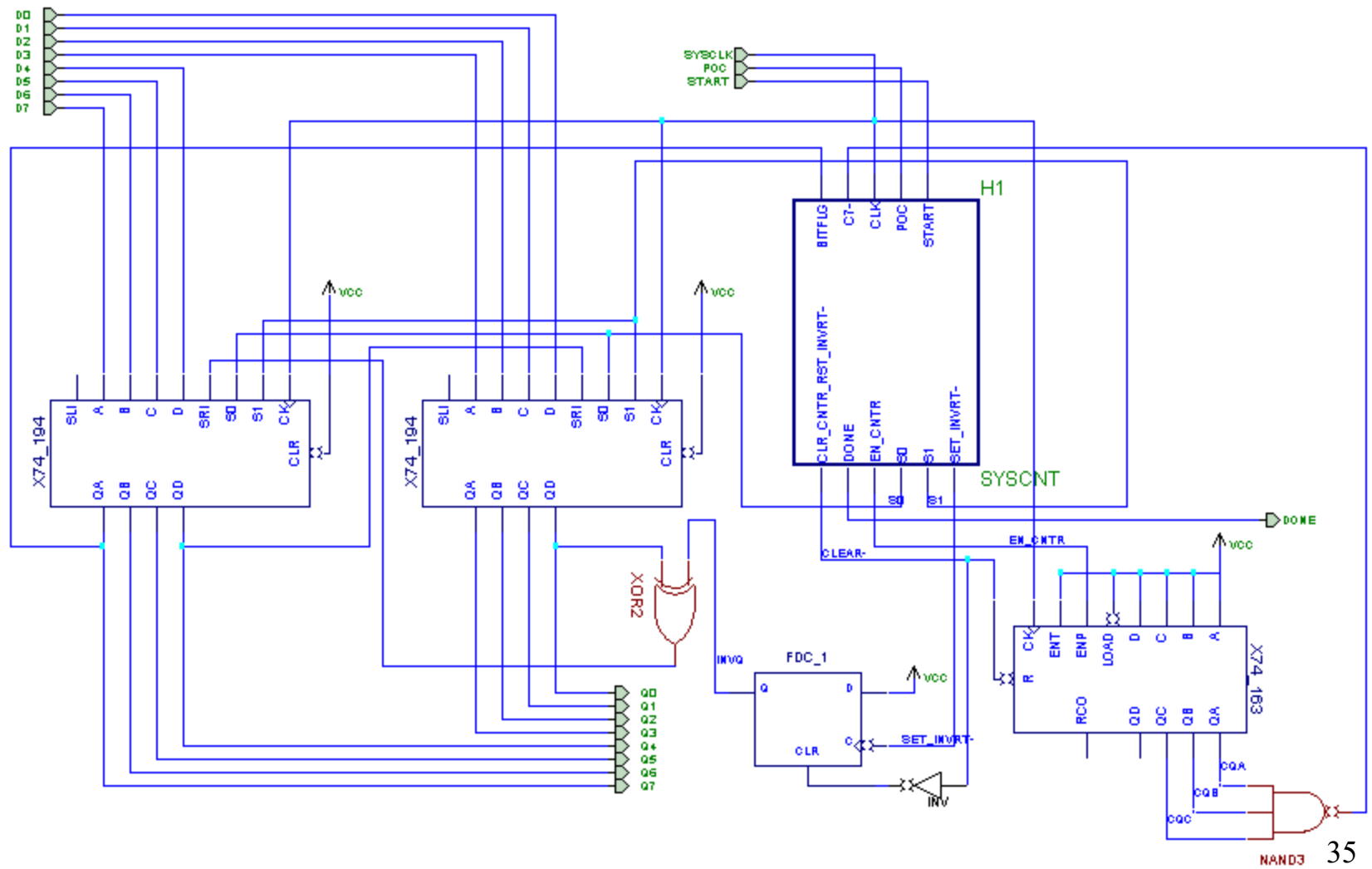

SYSCNT

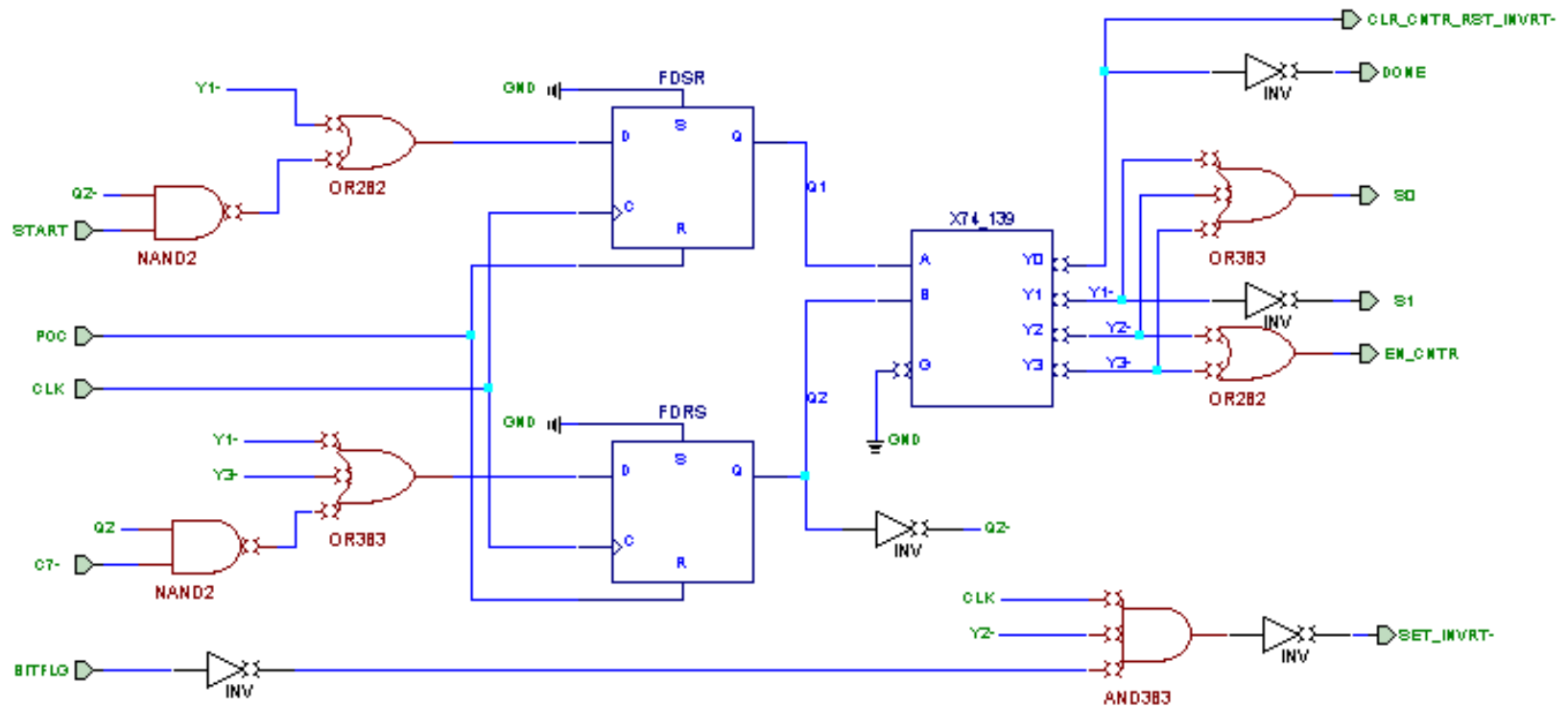

Hints

- **Sequential Two's complement machine**
 - Analyze a machine that takes the 2's complement of an 8-bit number
 - 8 bits in, START \rightarrow 8 bits out, DONE
 - More realistic example that uses MSI chips
 - For PLDs, FPGAs design, we usually use functional blocks (LBB – Logic Building Block) equivalent to the counters, shift registers, decoders, etc

General Architecture and Operation

- **Example: 01001010 \rightarrow 10110110 (2's complement of A = $2^n - A$)**
 - 01001010 \rightarrow 11111111+1 – 01001010 = 10110101 + 1 = 10110110
 - Write down bits from right until a 1 is encountered. Complements all bits there after
- **General Operation Flow**
 - Load 8 bits into 2 \times 74194 (4 bit shift right/left register)
 - Do a circular shift on the data, inverting bits as necessary
 - Finally, the 2's complement data will appear at the output after 8 shift operations

	Parallel Data Out Q ₇ Q ₆ Q ₅ Q ₄ Q ₃ Q ₂ Q ₁ Q ₀								Invert InvertQ
	-	-	-	-	-	-	-	-	0
	0	1	0	0	1	0	1	0	0
1	0	0	1	0	0	1	0	1	0
2	1	0	0	1	0	0	1	0	1
3	1	1	0	0	1	0	0	1	1
4	0	1	1	0	0	1	0	0	1
5	1	0	1	1	0	0	1	0	1
6	1	1	0	1	1	0	0	1	1
7	0	1	1	0	1	1	0	0	1
8	1	0	1	1	0	1	1	0	1

General Architecture and Operation


- **74LS194 (4 bit shift register) is used for loading & shifting 8 bit data**
- **We use D f/f (with asynchronous clear) to remember from when inverting is necessary**
- **We use 74LS163 (a synchronous 4-bit counter) to count 8 shifts**
- **System controller control the overall operation**
 - The system controller determines when data should be loaded, shifted or held by controlling S1 and S0
 - The system controller also looks at BITFLG so as to know when to set the INVERT D f/f
 - The system controller also clears 74LS163 at the beginning, increments it each time a bit is shifted, and detects when 8 bits have been shifted.
 - Finally, the system controller asserts DONE signal

Much larger system analysis

- **Analysis of the structure**
 - More than a few f/fs in circuit – not practical to treat as a single state machine
 - Try directly applying the 3-step approach
 - How many f/fs?
 - Shift reg – 8, Counter – 4, INVERT –1, System Controller –2
 - 15 f/fs $\Rightarrow 2^{15}$ states
- **Then, 3 step analysis only on system controller**


Synchronous System Structure

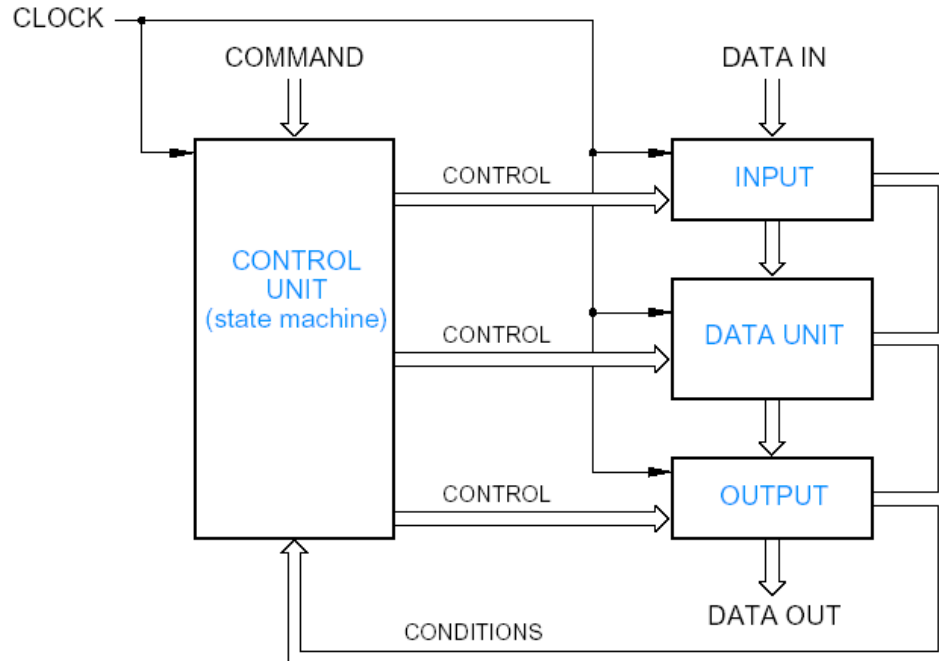
- **Generally 2 Parts: Data Unit & Control Unit**
 - Data unit: process data (store, route, combine)
 - Control unit: starting and stopping actions, test conditions, decide what to do next
 - Only control unit – designed as state machine



Decomposing State Machines

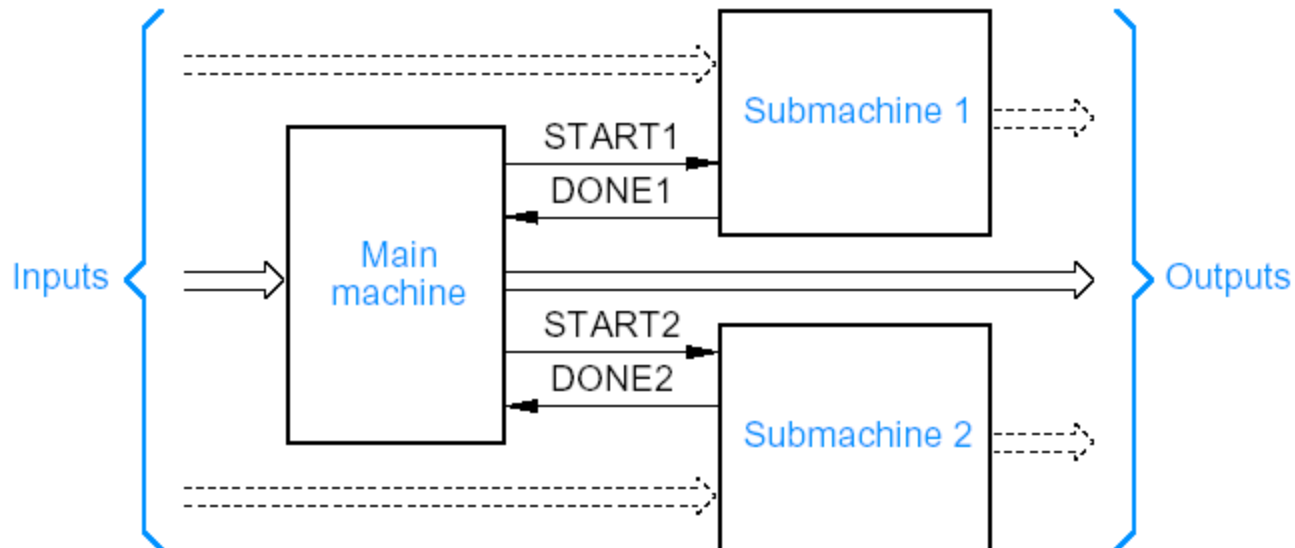- **The control unit may be further partitioned**
 - Main machine – system controller
 - Sub machines – counter, INVERT D f/f




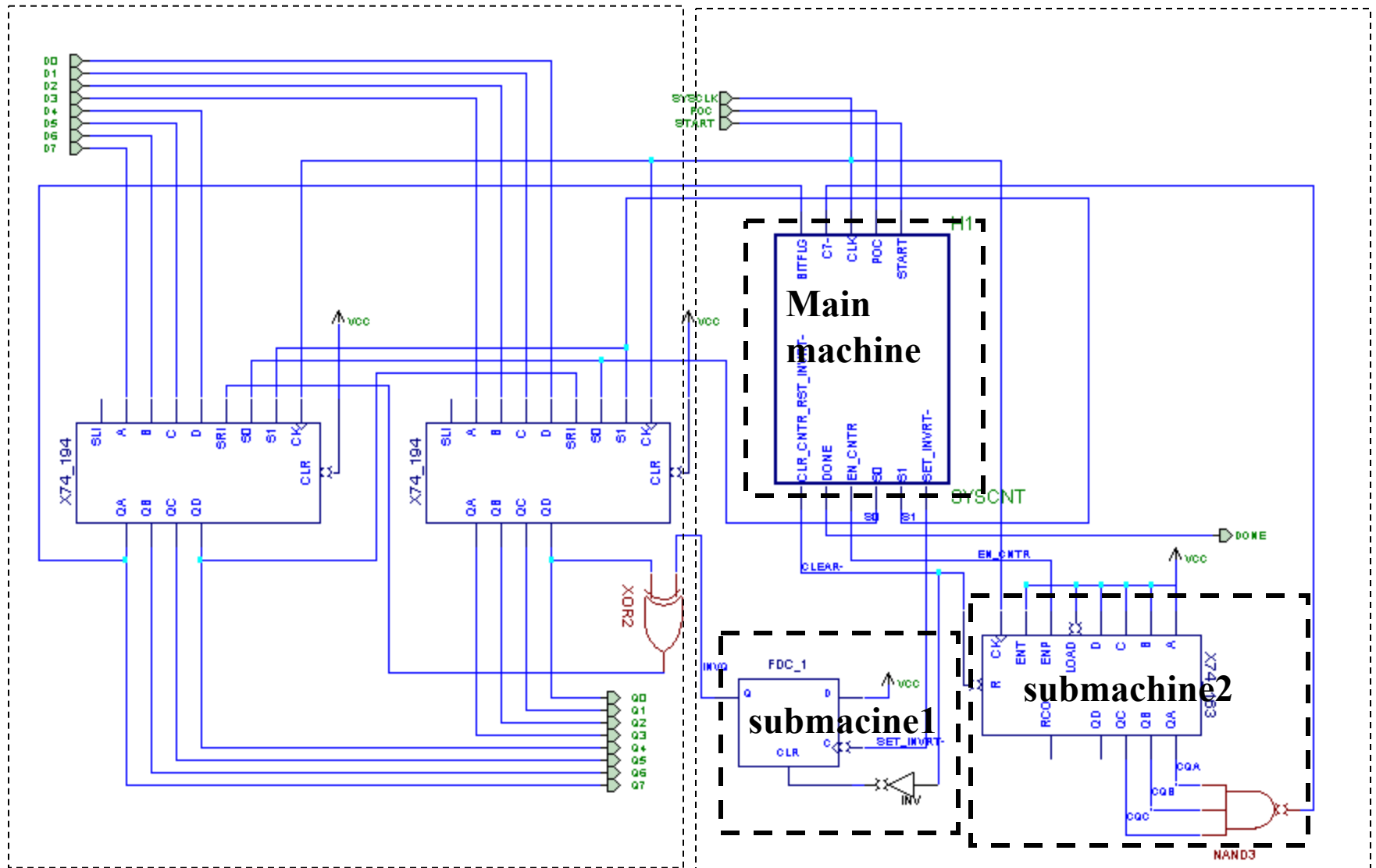

Data unit

Control unit (State Machine) 44

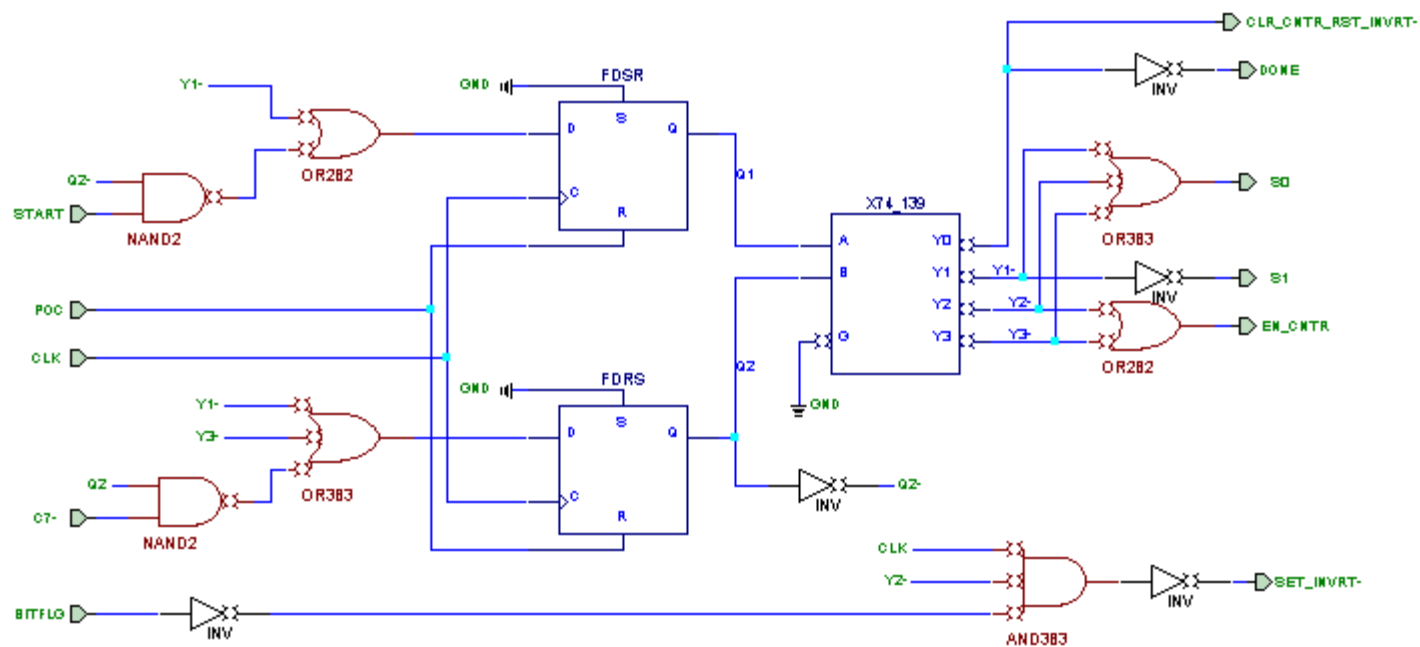**Do a 3 step analysis only on
system controller**



Step 1: Excitation and Output Eqs.

• Inputs?

- External inputs (4): CLK, START, BITFLAG, C7 (ignore POC for simplification)
- P.S. (2): Q1, Q2

• Outputs?

- External outputs (7): CLR_CNTR, RST_INVRT, S0, S1, ENCNTR, SET_INVRT, DONE
- N.S. (2): = Excitations D1, D2

$$D_2 = Y_1 + Y_3 + Q_2 \bar{C}_7 = Q_1 + Q_2 \bar{C}_7$$

$$D_1 = Y_1 + \bar{Q}_2 START = \bar{Q}_2 Q_1 + \bar{Q}_2 START$$

$$ENCNTR = Y_3 + Y_2 = Q_2$$

$$S_1 = Y_1 = \bar{Q}_2 Q_1$$

$$S_0 = Y_3 + Y_2 + Y_1 = Q_2 + Q_1$$

$$DONE = Y_0 = \bar{Q}_2 \bar{Q}_1$$

$$CLR_CNTR = \bar{Q}_2 \bar{Q}_1$$

$$RST_INVRT = \bar{Q}_2 \bar{Q}_1$$

$$SET_INVRT = \overline{CLK \cdot Y \cdot BITFLAG} = \overline{CLK \cdot Q_2 \bar{Q}_1 \cdot BITFLAG}$$

Why falling edge of CLK?

Can we remove CLK from SI equation? → No

1. avoid glitch on SI when transit to Y2

2. hold time on RIN (not likely the problem)

Step 2: State/Output Table

- **How many rows and columns?**

P.S.		Inputs					Outputs							N.S.		
Q2	Q1	START	BFLAG	C7			EC	CC	S1	S0	RI	SI	DONE	Q2(=D2)	Q1(=D1)	
{ 32 rows																

Step 2: State/Output Table

- Variable entered table**

P.S.		Outputs							N.S.	
Q2	Q1	EC	CC	S1	S0	RI	SI	DONE	Q2	Q1

$$D_2 = Y_1 + Y_3 + Q_2 \overline{C_7} = Q_1 + Q_2 \overline{C_7}$$

$$D_1 = Y_1 + \overline{Q_2} START = \overline{Q_2} Q_1 + \overline{Q_2} START$$

$$ENCNTR = Y_3 + Y_2 = Q_2$$

$$S_1 = Y_1 = \overline{Q_2} Q_1$$

$$S_0 = Y_3 + Y_2 + Y_1 = Q_2 + Q_1$$

$$DONE = Y_0 = \overline{Q_2} \overline{Q_1}$$

$$CLR_CNTR = \overline{Q_2} \overline{Q_1}$$

$$RST_INVRT = \overline{Q_2} \overline{Q_1}$$

$$SET_INVRT = \overline{CLK} \cdot Y \cdot BITFLAG = \overline{CLK} \cdot Q_2 \overline{Q_1} \cdot BITFLAG$$


Step 2: State/Output Table

- Variable entered table

	P.S.		Outputs							N.S.	
	Q2	Q1	EC	CC	S1	S0	RI	SI	DONE	Q2	Q1
Y0	0	0	0	1	0	0	1	0	1	0	ST
Y1	0	1	0	0	1	1	0	0	0	1	1
Y3	1	1	1	0	0	1	0	0	0	1	0
Y2	1	0	1	0	0	1	0	↑	0	$\overline{C_7}$	0

$\overline{CLK} \cdot BITFLG$

Step 3: State Diagram

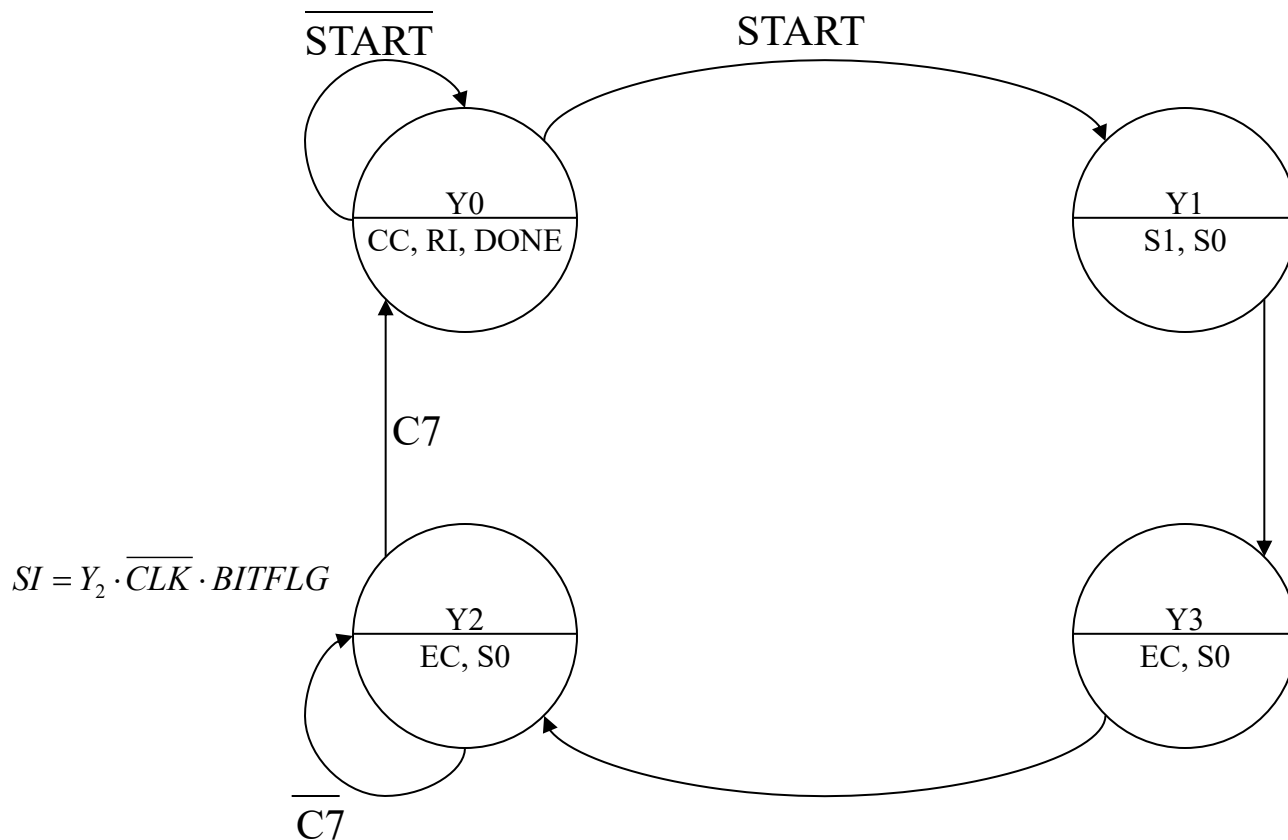

Quiz: Why we need Y3? Can we merge it with Y2?


Example

	Shift register	State	Counter	Invert
START →	XXXXXX	Y0	-	-
	XXXXXX	Y1	0	0
	11001010	Y3	0	0
	01100101	Y2	1	0
	10110010	Y2	2	0->1
	11011001	Y2	3	1
	01101100	Y2	4	1
	10110110	Y2	5	1
	11011011	Y2	6	1
	01101101	Y2	7	1
	00110110	Y0	8	1
	00110110	Y0	0	0

→
DONE

Sample Timing Diagram

Parallel Data In = 0100 1010

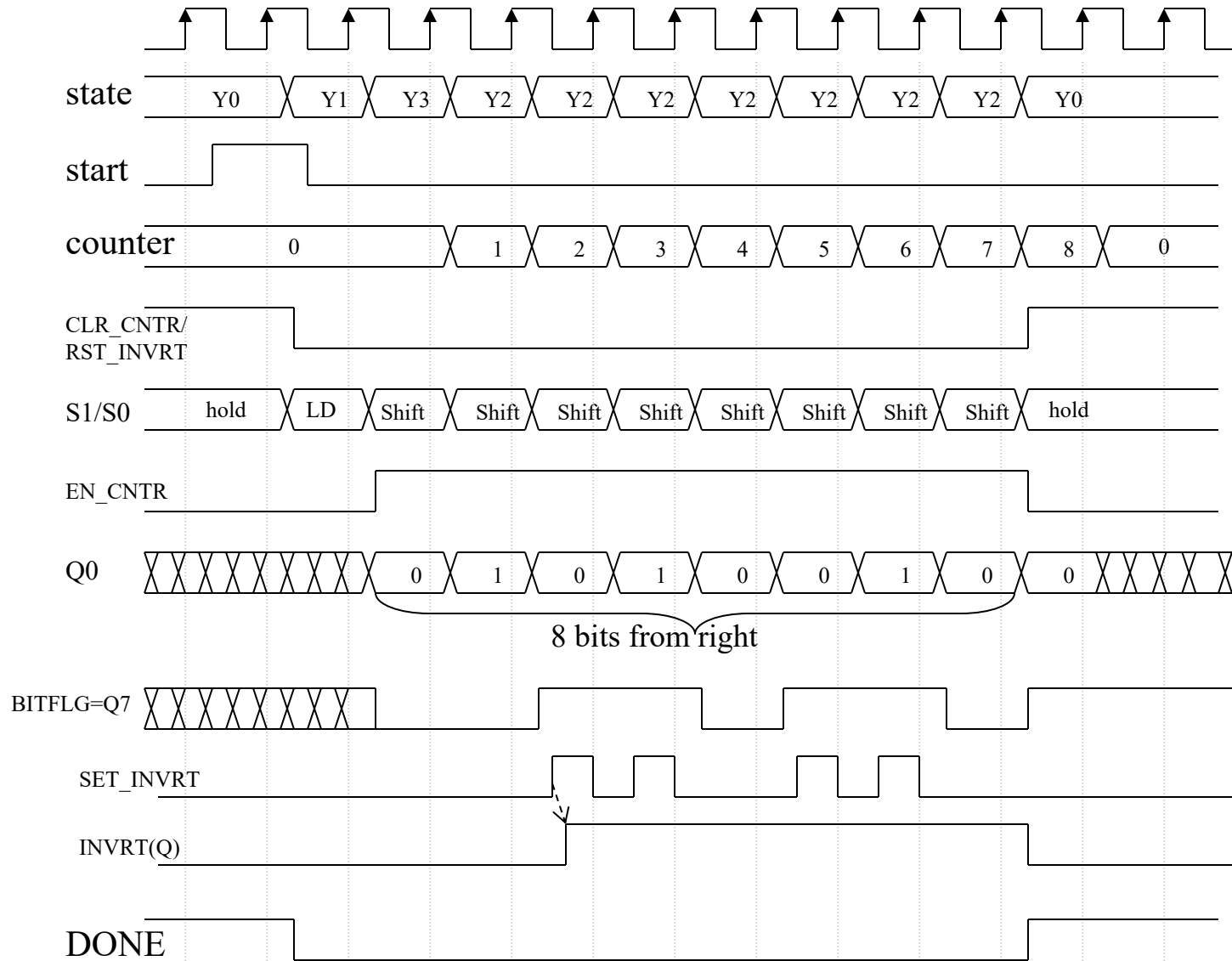

Timing Analysis

- Timing specs. for the parts we have used

Chip	tpLH(ns)	tpHL(ns)
LS00(2NAND), LS04(INV), LS10(3NAND), LS27(3NOR)	15	15
LS86(2XOR)	30	22
LS139 A,B -> Y	29	38
LS139 G -> Y	24	32

LS74 (Dff)	tpLH	tpHL	ts	th
CLR, CLK, PR->Q	25	40		
D			20	5
fmax = 25 Mhz				

LS163 (Counter)	tpLH	tpHL	ts	th
CLK->Q	24	27		
CLK->RCO	35	35	20	5
ENT->RCO	14	14		
CLR->Q		28		
A,B,C,D,ENP,ENT, LD			20	0
fmax = 25 Mhz				

LS194 (Sft Register)	tpLH	tpHL	ts	th
CLR->Q		35		
CLK->Q	26	30		
S1, S0			30	
L,R,A,B,C,D			20	
All				0
fmax = 25 Mhz				

Maximum CLK frequency

- We must satisfy setup time for all f/f inputs (we will consider only D2, S0, RIN as examples)**

D2 setup	Path1: <u>CLK→Q2(LS74)</u> + <u>B→Y3(LS139)</u> + <u>Y3→D2(LS10)</u> + D2_setup = 40+38+15+20=113ns
	Path2: <u>CLK→Q2(LS74)</u> + <u>LS00</u> + <u>LS10</u> + D2_setup = 40+15+15+20=90ns
	Path3: <u>CLK→CNTR_Q(LS163)</u> + <u>CNTR_Q→C7(LS10)</u> + <u>LS00</u> + <u>LS10</u> + D2_setup = 27+15+15+15+20=92ns
S0 setup	Path1: <u>CLK→Q2,Q1(LS74)</u> + <u>A,B→Y(LS139)</u> + <u>Y→S0(LS10)</u> + S0_setup = 40+38+15+30=123ns
RIN (=SRI: Shift Right Input) of Left 'x194' setup	Path1: <u>CLK→Q0(LS194)</u> + <u>LS86</u> + RIN_setup = 30+30+20=80ns
	Path2: <u>CLK(falling edge)→SI (LS27,LS04)</u> + <u>SI→INVQ(LS74)</u> + <u>LS86</u> + RIN_setup = 15+15+25(40?)+30+20=105(120?)ns → ½ tclk > 105(120?)ns → 210(240?)ns


$$\text{Max clk frequency} = 1/210\text{ns} = 4.8\text{Mhz}$$

If we use the pure maximum value approach,

$$\text{Max clk frequency} = 1/240\text{ns} = 4.2\text{Mhz}$$

Setup and Hold time specifications on START

- t_s for START**

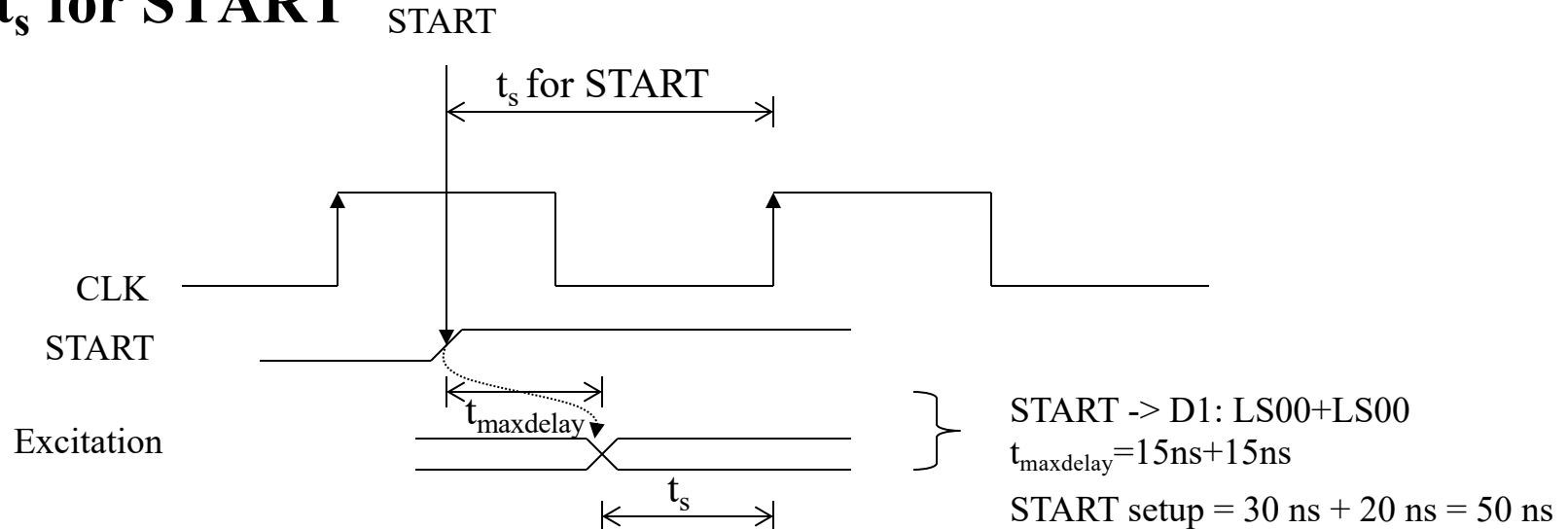

- t_h for START**

